

UNIT II: Combinational Logic

FACULTY

**Dr. K. ARTHI MCA, M.Phil., Ph.D.,
Assistant Professor,
Postgraduate Department of Computer Applications,
Government Arts College (Autonomous),
Coimbatore-641018.**

Introduction to ALU

- ALU stands for: **A**rithmetic **L**ogic **U**nit
- ALU is a digital circuit that performs Arithmetic (Add, Sub, . . .) and Logical (AND, OR, NOT) operations.
- John Von Neumann proposed the ALU in 1945 when he was working on EDVAC.

Introduction to ALU (contd...)

- An ALU is the fundamental unit of any computing system.
- Understanding how an ALU is designed and how it works is essential to building any advanced logic circuits.
- Using this knowledge and experience, we can move on to designing more complex integrated circuits.
- The ALU is the “heart” of a processor—you could say that everything else in the CPU is there to support the ALU.

Typical Schematic Symbol of an ALU


A and B: the inputs to the ALU
(aka operands)

R: Output or Result

F: Code or Instruction from the
Control Unit (aka as op-code)

D: Output status; it indicates cases
such as:

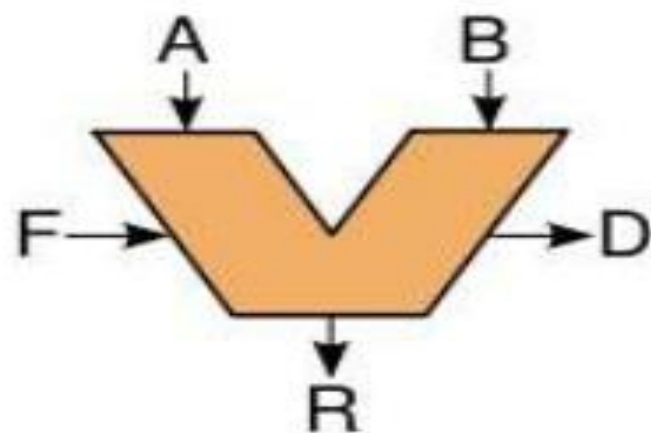- carry-in
- carry-out,
- overflow,
- division-by-zero
- And . . .



TYPES OF DIGITAL LOGIC CIRCUITS IN ALU

- COMBINATIONAL CIRCUITS
- SEQUENTIAL CIRCUITS

INTRODUCTION TO COMBINATIONAL CIRCUITS

- Combinational Circuits are made of logic gates.
- Doesn't contain memory element, that's why they can't store any information.
- Value of present output is determined by present input.
- Examples of combinational circuits are half adders, full adders, subtractors etc.

Combinational Circuits



- Binary values of outputs are a function of binary combination of inputs
- Outputs at any given time are entirely dependent on inputs that are present at that time


Adding 2 Numbers

- Write the truth table for addition of 2 bits A & B


A	B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Write Boolean representation for Sum & Carry
 - $S = A/B + AB' = A \oplus B$
 - $C = AB$

Combinational Circuits Based ALU

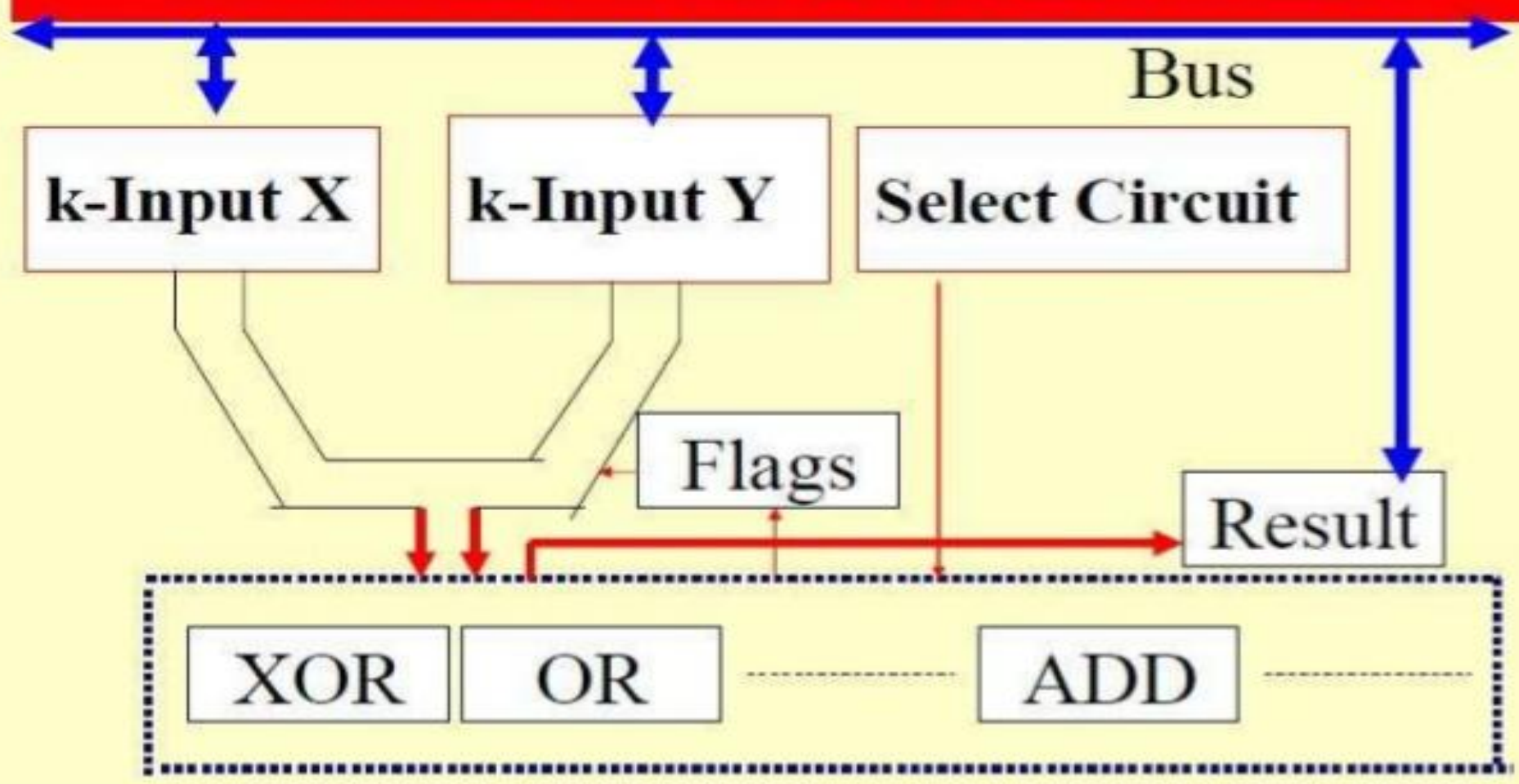

AN ALU USING COMBINATIONAL CIRCUITS

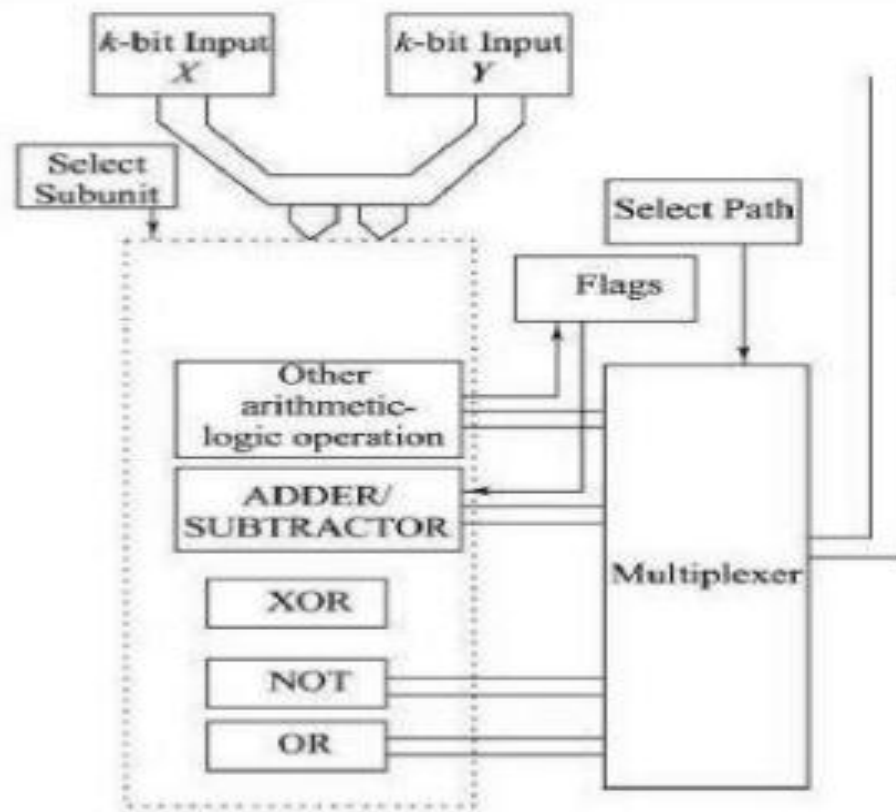


Examples of Combinational Circuits:

- Multiplexer
- Demultiplexer
- Encoder
- Decoder
- Half Adder
- Full Adder

Multiplexer & Demultiplexer

- Multiplexer-
 - A multiplexer is a combinational circuit where binary information from one of many input lines is selected and directs it to a single output line.
- Demultiplexer-
 - Demultiplexing is the reverse process of multiplexing; i.e., a demultiplexer is a combinational circuit that receives information on a single line and transmits this information on one of 2^n possible output lines.

Multiplexer

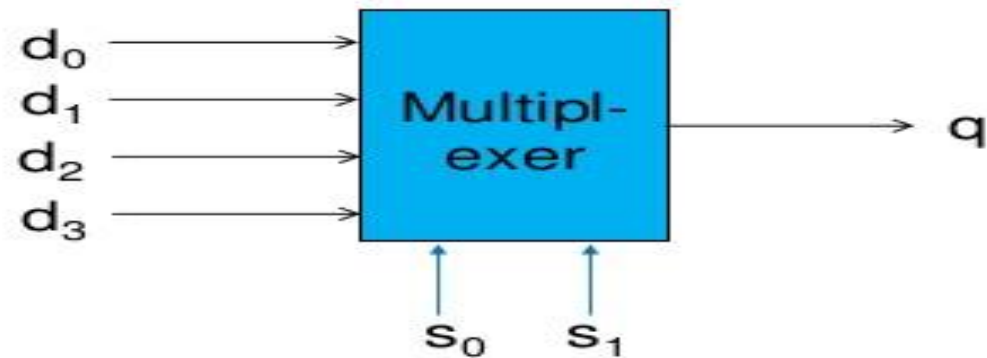

- ❑ Receives binary data from 2^n lines & connect them to a single output line based on a selection
- ❑ By applying a control signals we can steer any input to the output


Multiplexer (Cont.)

□ Truth table


s_0	s_1	q
0	0	d_0
0	1	d_1
1	0	d_2
1	1	d_3

Multiplexer (Cont.)


Logic circuit

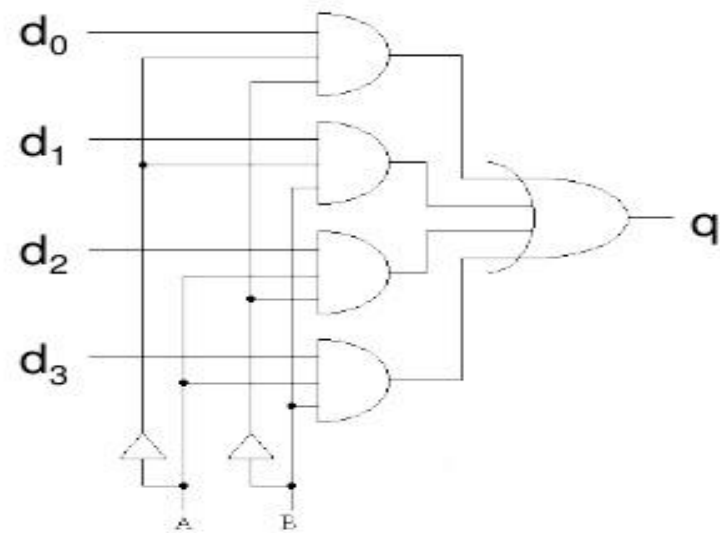

8-to-1 Multiplexer

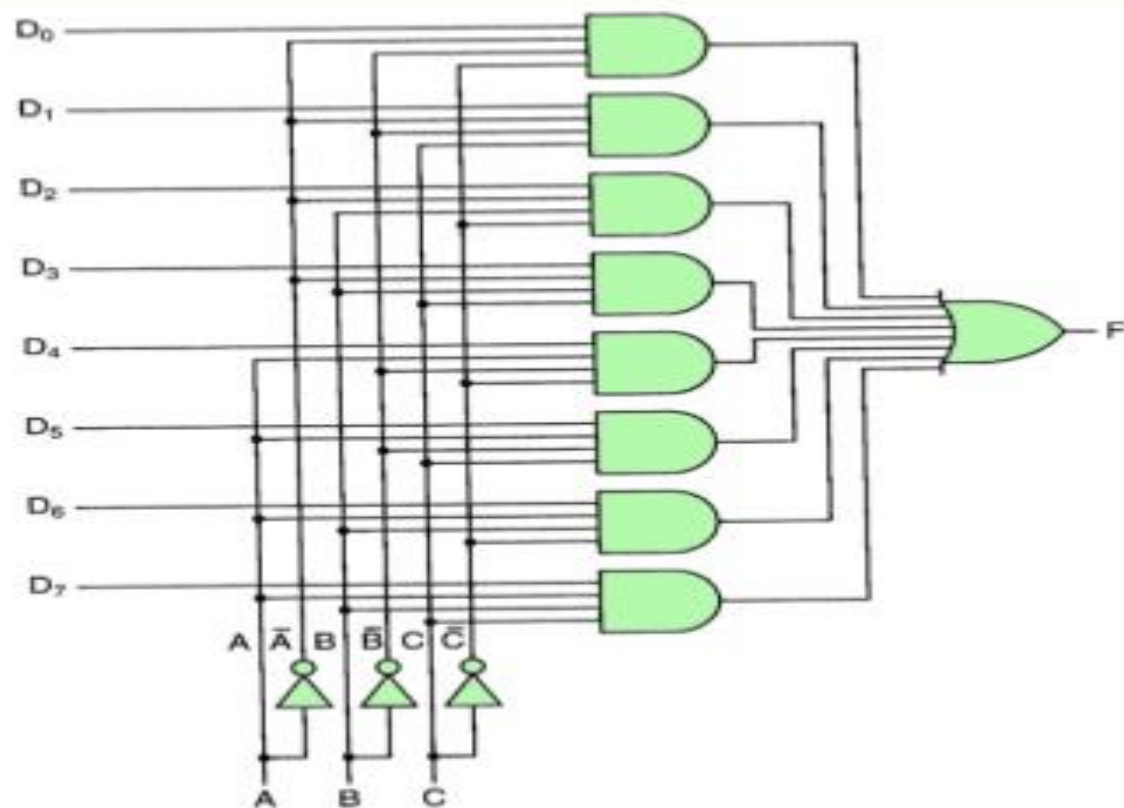


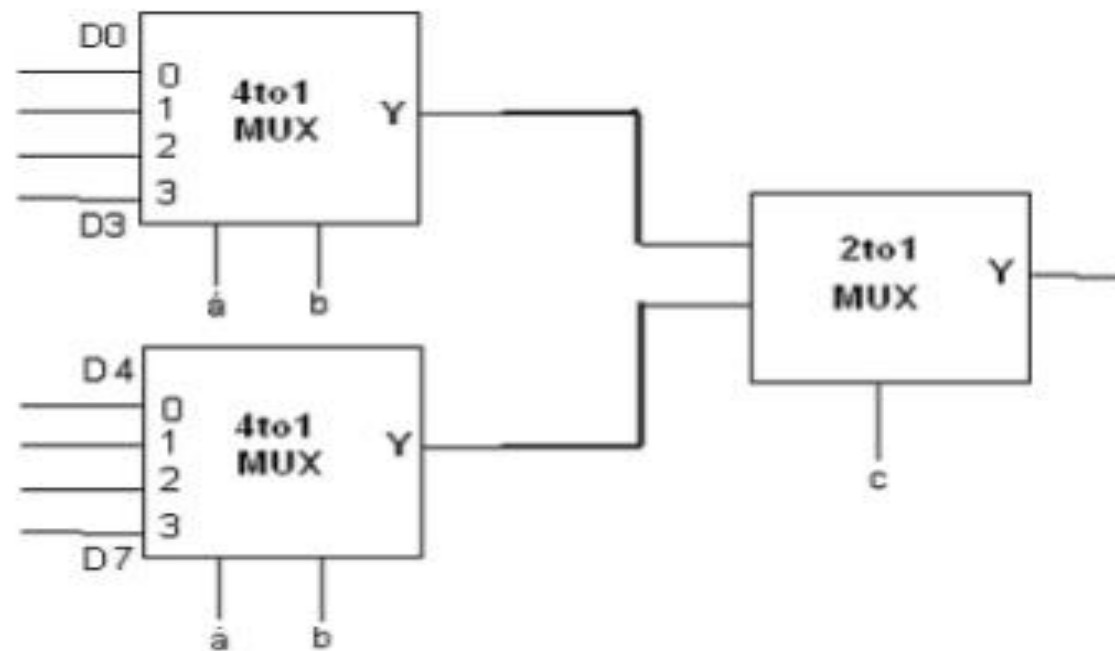8-to-1 Multiplexer using 4-to-1 & 2-to-1 Multiplexers



Source: www.exploreroots.com/dc28.html

Demultiplexer

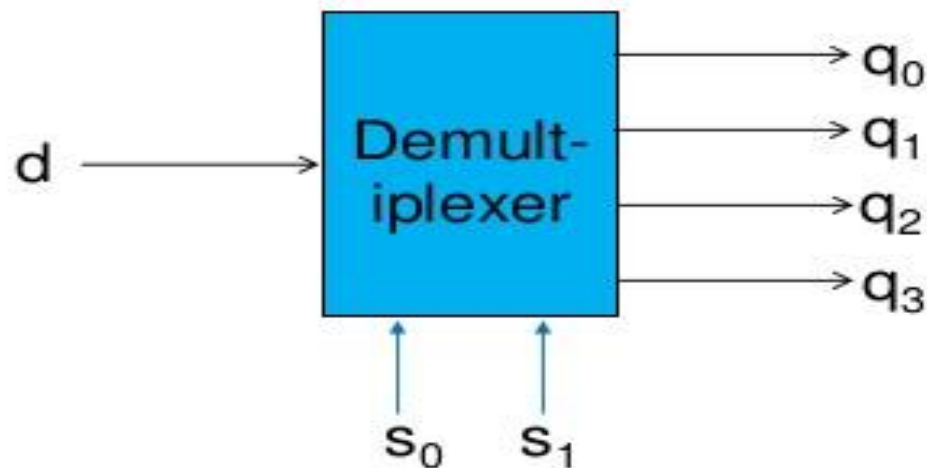


- Reverse process of a multiplexer
- By applying a control signals we can steer the input signal to one of the output lines

Demultiplexer (Cont.)


Truth table

s_0	s_1	q_0	q_1	q_2	q_3
0	0	d			
0	1		d		
1	0			d	
1	1				d

Logic circuit

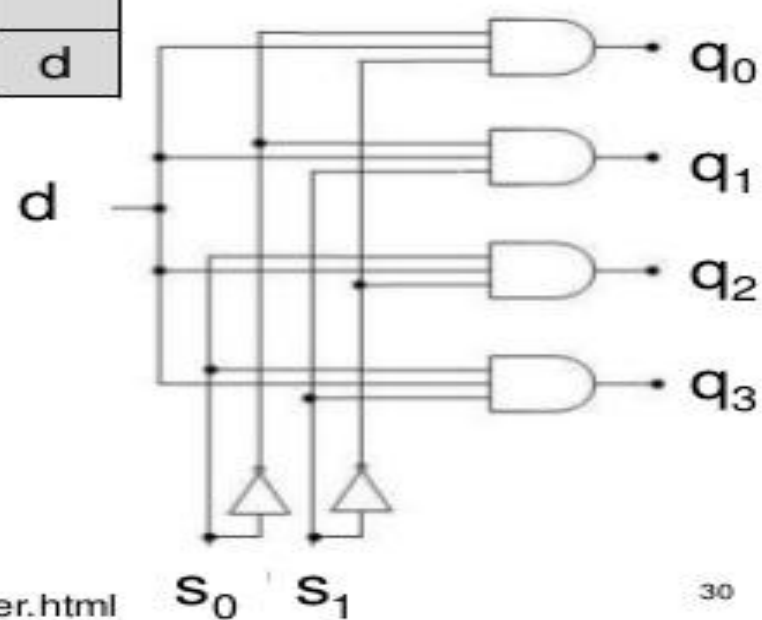


Demultiplexer Using Decoder

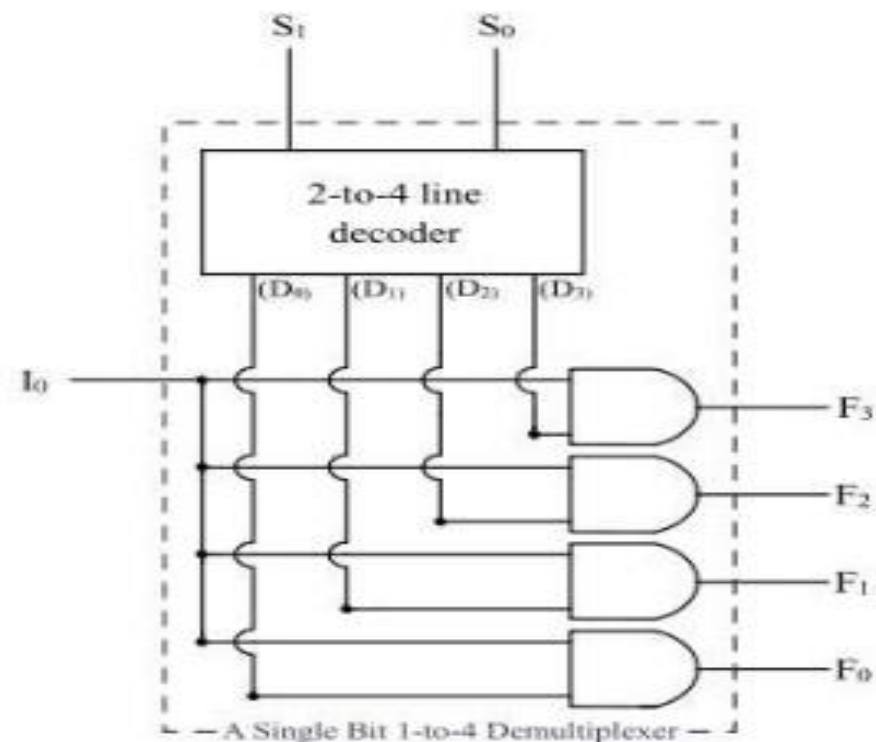

Source: <http://en.wikipedia.org>

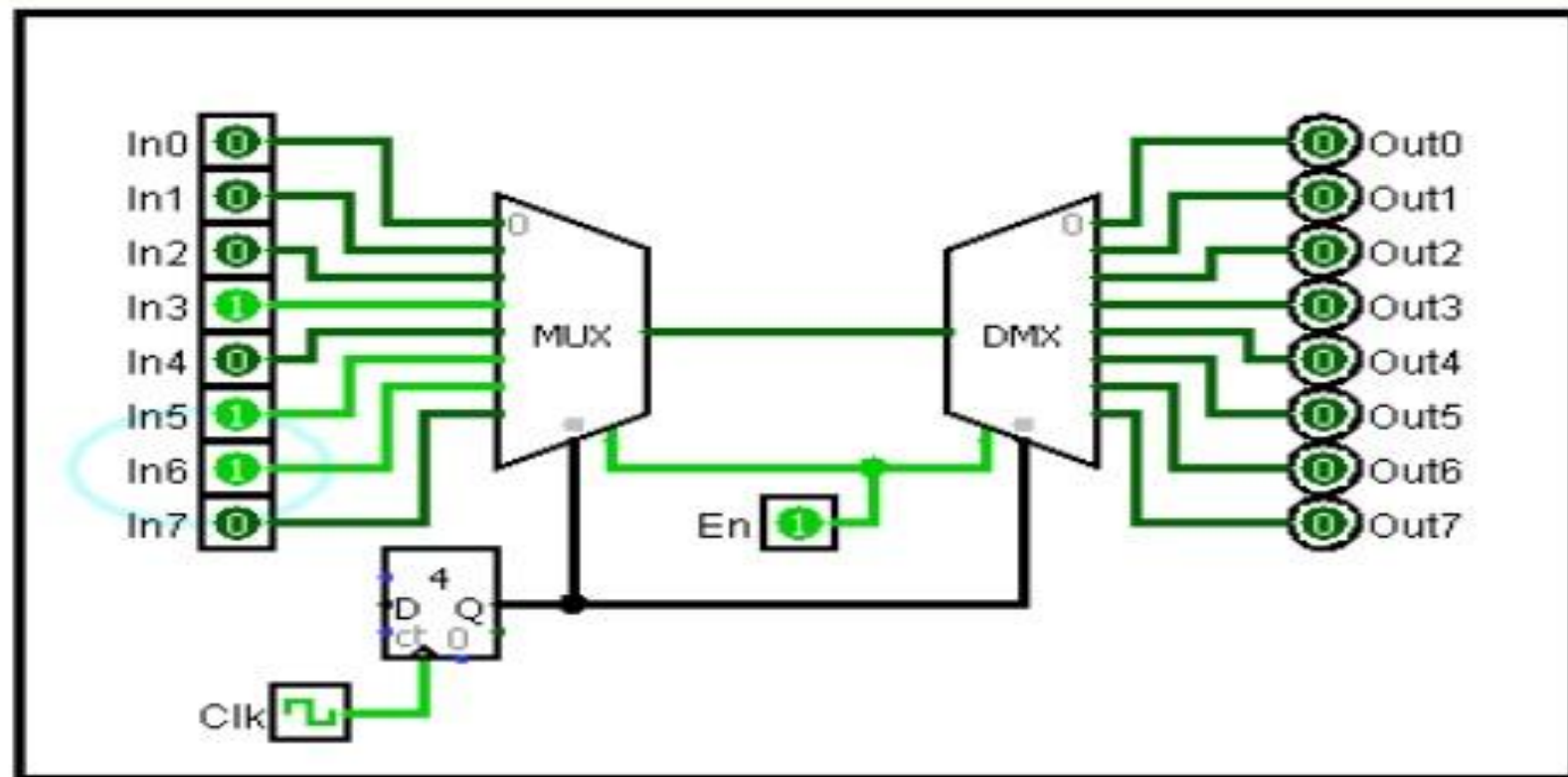Multiplexer/Demultiplexer - Application in Telecommunication



Source: <http://digilogwiki.com/index.php?title=Multiplexers/Demultiplexers>

Encoder & Decoder

- Encoder-
 - An encoder is a combinational circuit that produces the reverse function from that of a decoder.
- Decoder-
 - A decoder is a combinational logic circuit that receives coded information on n input lines and feeds them to maximum of 2^n unique output lines after conversion.

Decoders

- Suppose a simple microprocessor supports following 2 instructions

- ADD

$R_c = R_a + R_b;$
 $PC = PC + 1;$

0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	Ra			Rb			Rc			0	0	0	0	0


- LOAD

$R_a = d;$
 $PC = PC + 1;$

0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
1	0	Ra			0 0 0			d							

- When these instructions execute they'll need to activate different circuits
 - Which circuit is determined by 2 most significant bits

Decoders

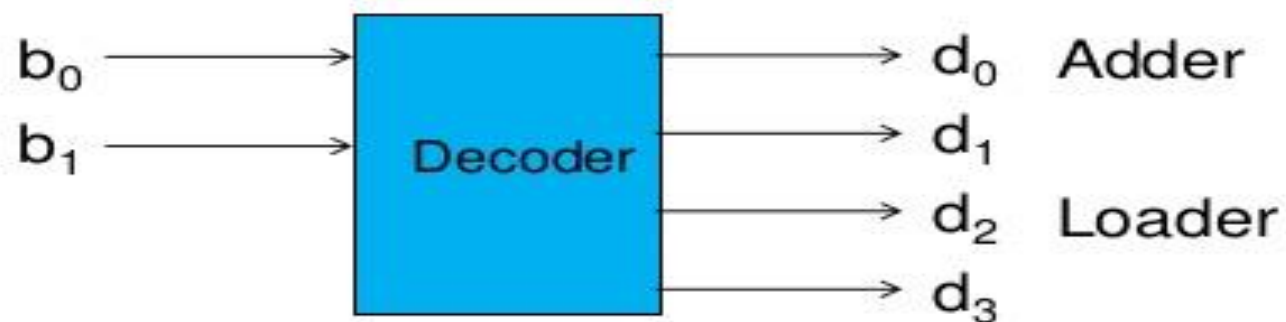

- ❑ Converts binary data from n coded inputs to a maximum of 2^n unique outputs
- ❑ Called n -to- 2^n decoder


Decoders

- Truth table for a 2-to-4 decoder

b₀	b₁	d₀	d₁	d₂	d₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1



Decoders

- Draw logic circuit of a 2-to-4 decoder

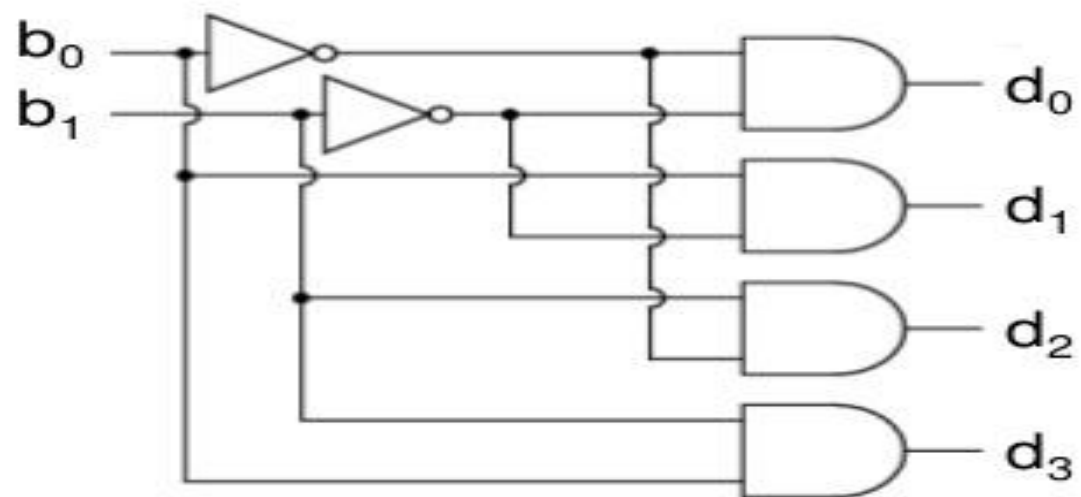


Source: www.allaboutcircuits.com/vol_4/chpt_9/4.html

3-to-8 Decoder

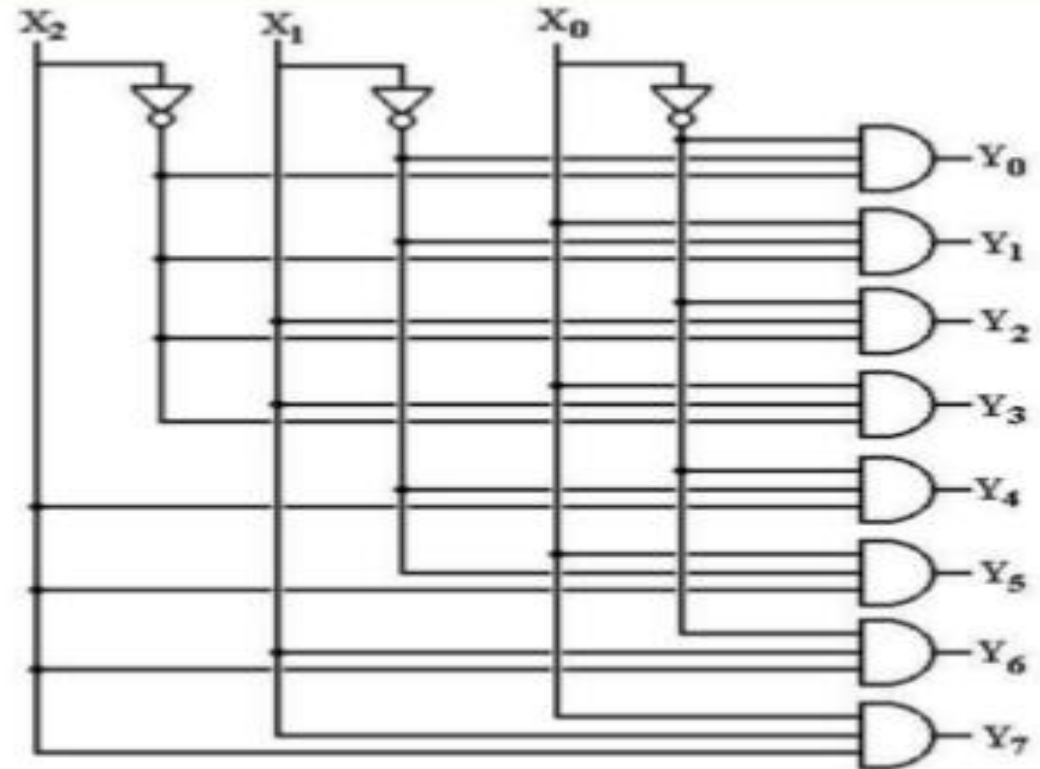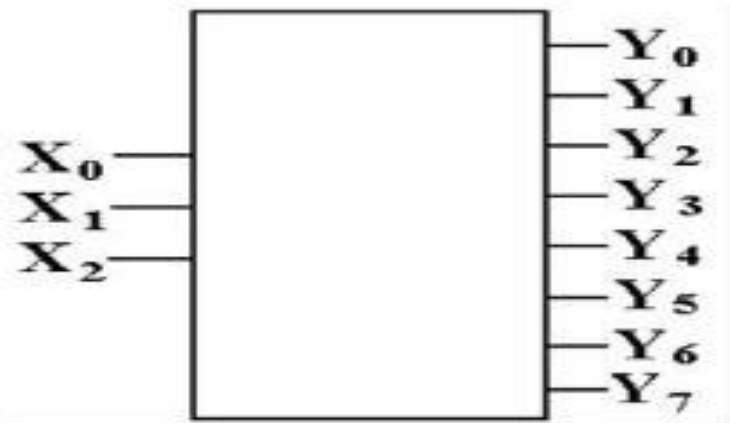


Decoder Expansion

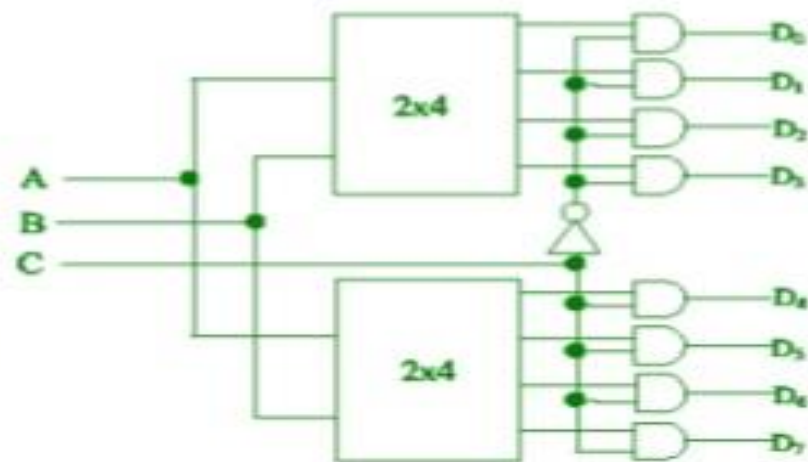- Build a 3-to-8 decoder using 2-to-4 decoders



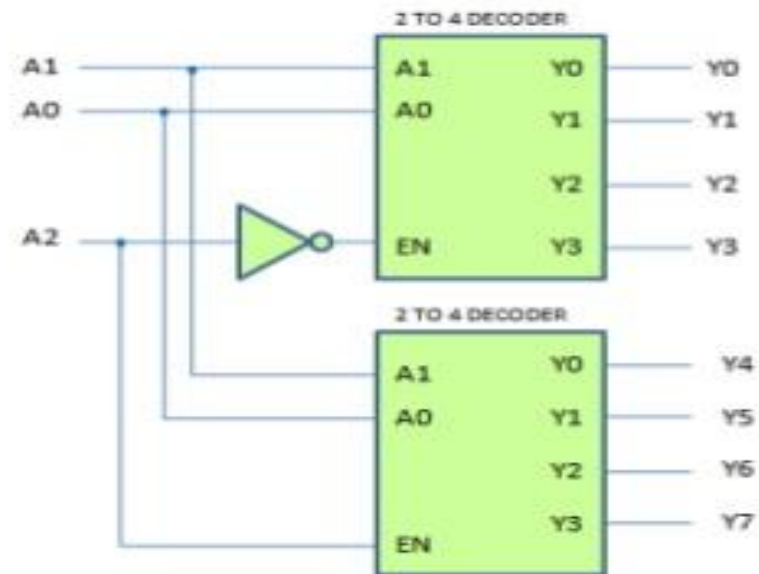Source: <http://dc167.4shared.com/doc/or00nekd/preview.html>



Source: www.teachurselfece.com/2012/02/decoders.html

Decoders (Cont.)

■ ADD


	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
$R_c = R_a + R_b;$ $PC = PC + 1;$	0	0	Ra			Rb			Rc			0	0	0	0	0

■ LOAD

	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
$R_a = d;$ $PC = PC + 1;$	1	0	Ra			0	0	0	d							


- Also helps us select which registers to use

Use of Decoders Inside CPU

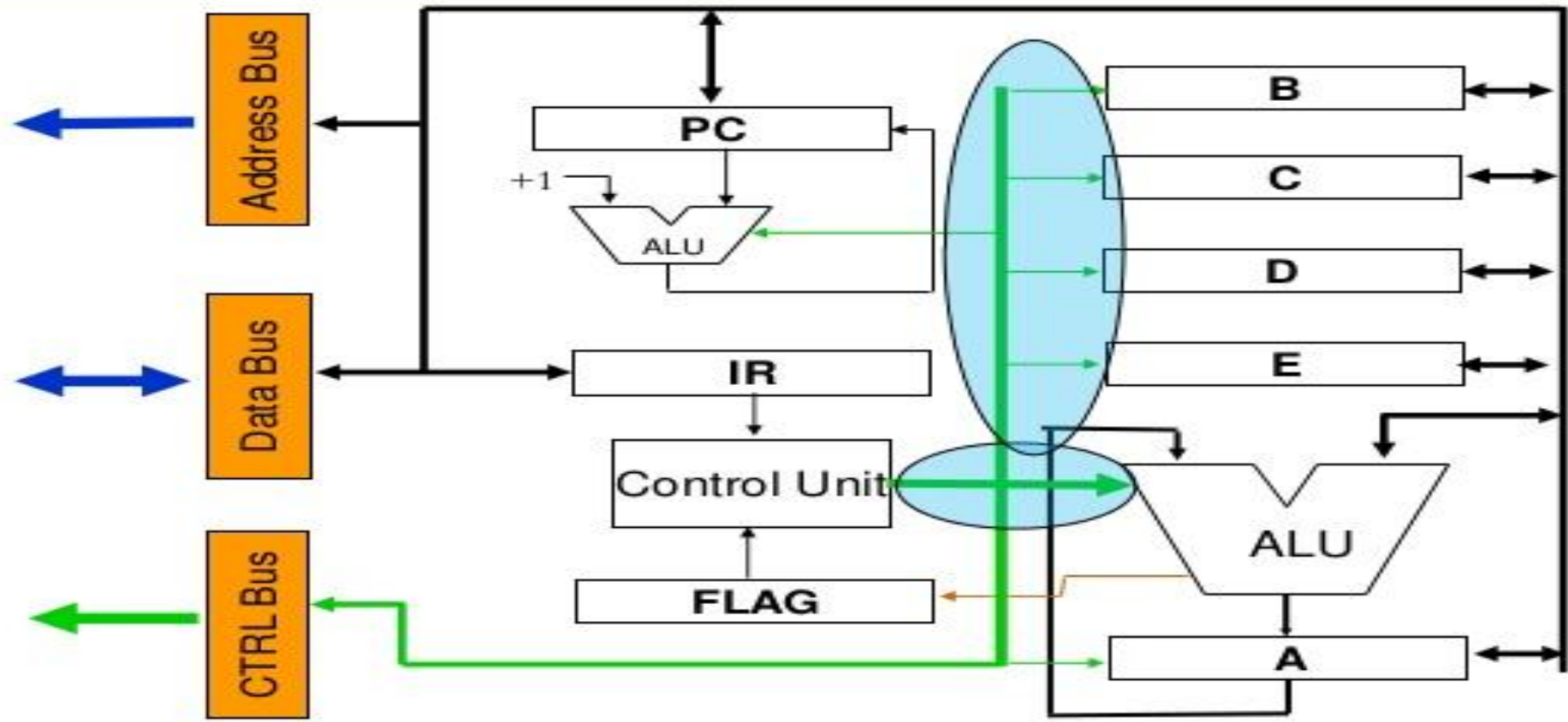

Encoders

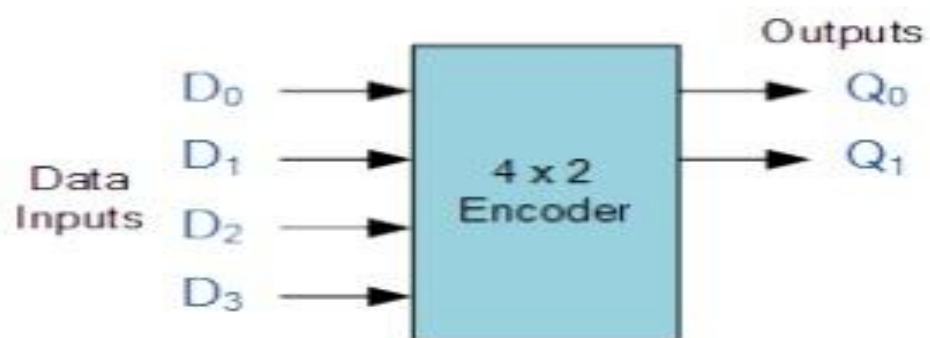- Reverse process of a decoder
 - 4-to-2 encoder
 - 3-to-8 encoder




Inputs				Outputs	
D_3	D_2	D_1	D_0	Q_1	Q_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


Source: www.electronics-tutorials.ws/combinational/comb_4.html

Encoders

- Draw logic circuit of a 4-to-2 encoder

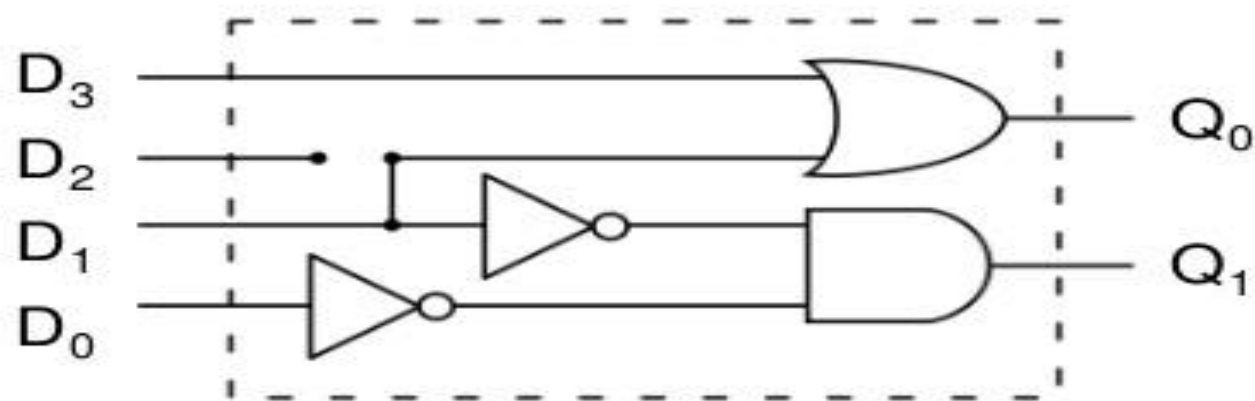

Priority Encoder

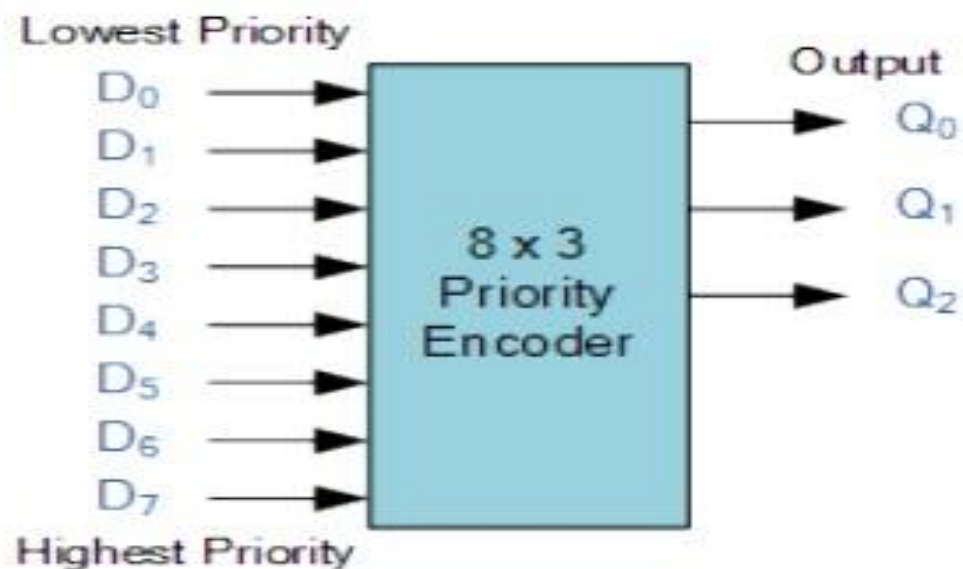


Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	x	0	0	1
0	0	0	0	0	1	x	x	0	1	0
0	0	0	0	1	x	x	x	0	1	1
0	0	0	1	x	x	x	x	1	0	0
0	0	1	x	x	x	x	x	1	0	1
0	1	x	x	x	x	x	x	1	1	0
1	x	x	x	x	x	x	x	1	1	1


X = dont care

Source: www.electronics-tutorials.ws/combination/comb_4.html

Internal Structure

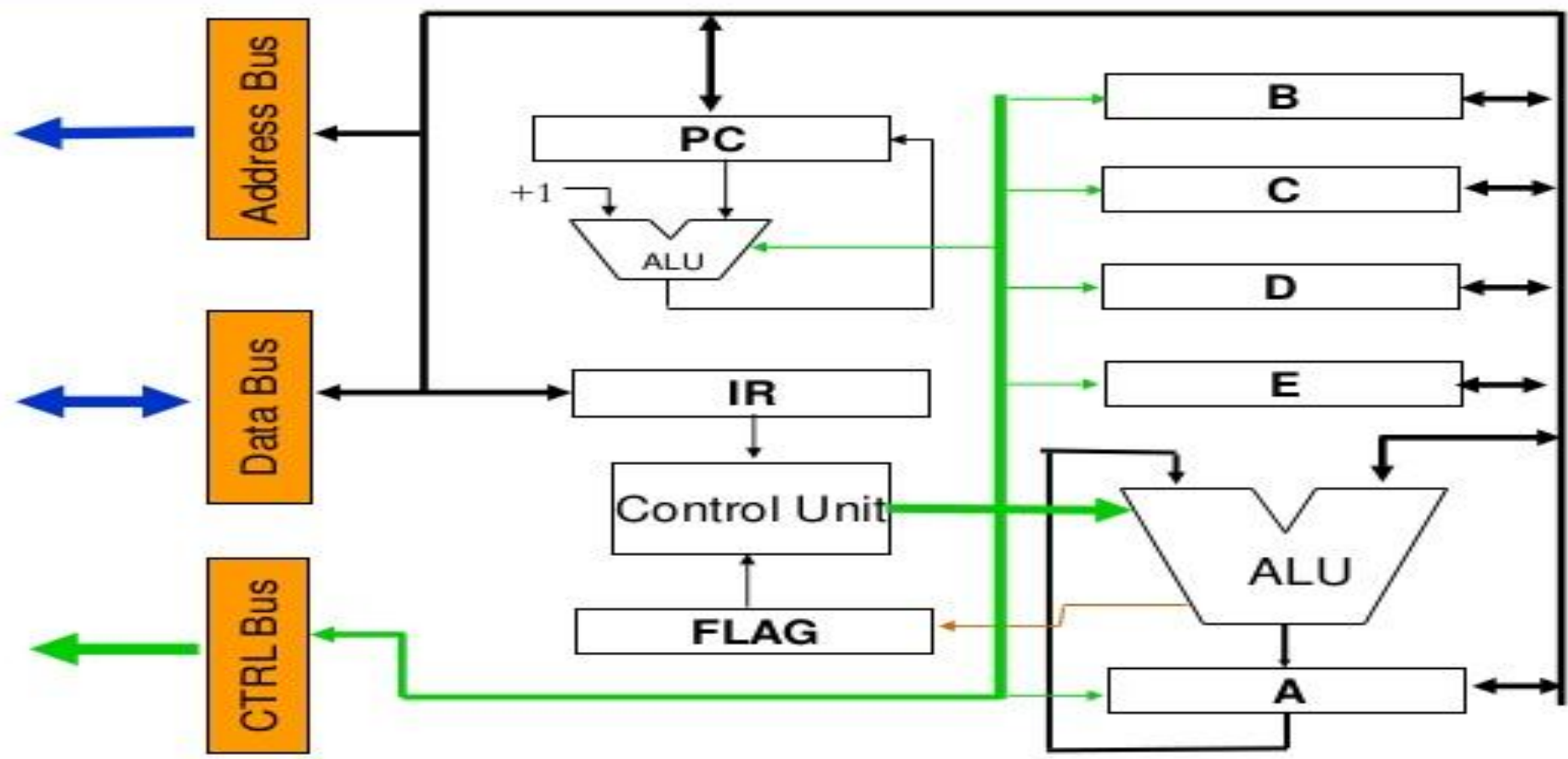

Internal Structure (Cont.)

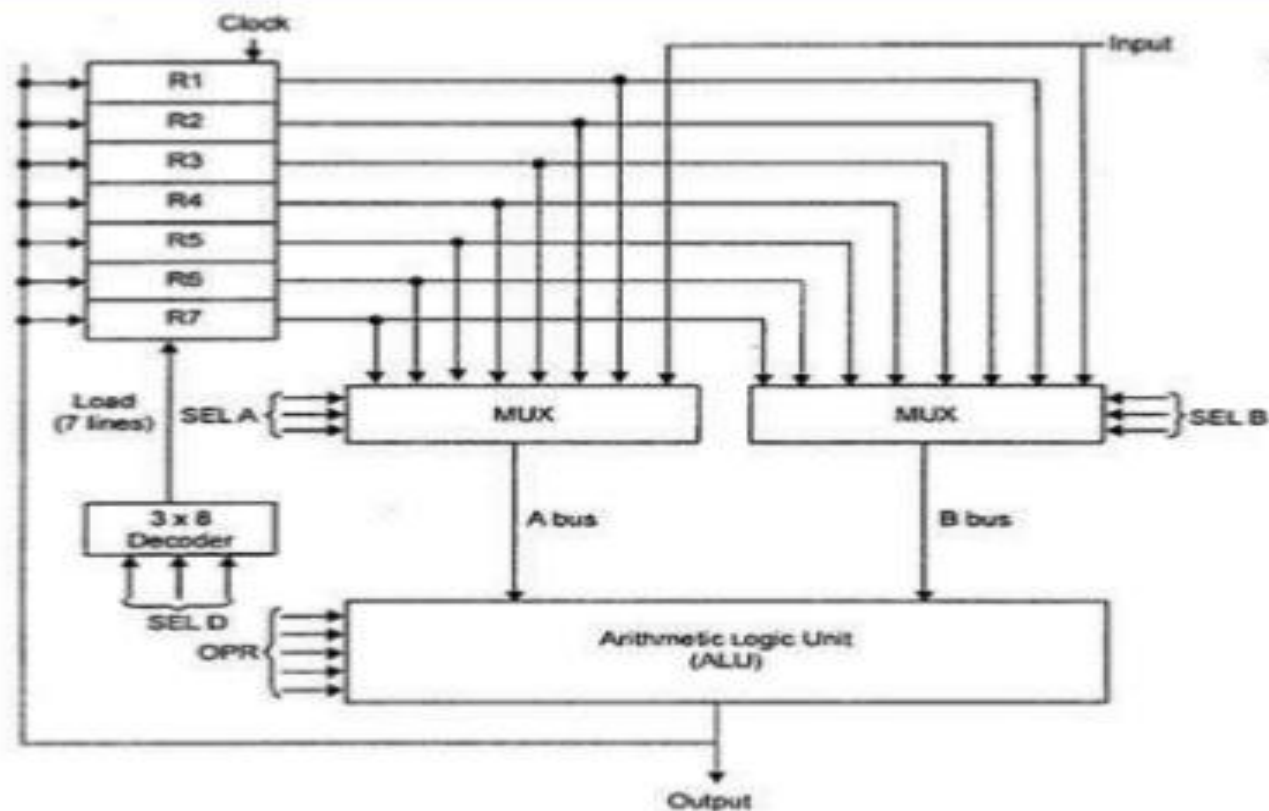

Source: www.transutors.com/homework-help/computer-science/computer-architecture/cpu/general-register-organization/

Half-Adder & Full-Adder

- Half-Adder :
 - A half-adder is a combinational circuit that performs the addition of two bits.
- Full Adder :
 - This type of adder is a little more difficult to implement than a half-adder.
 - The main difference between a half-adder and a full-adder is that the full-adder has three inputs and two outputs.

Adding 2 Numbers (Cont.)

- Draw logic circuit



Source: Wikipedia.org

- This is called a half adder

Adding 2 Numbers & a Carry

- Write the truth table for addition of 2 bits A & B as well as a carry from previous low-order bit

A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Adding 2 Numbers & a Carry (Cont.)

Write Boolean representation for Sum & Carry

- Hint – use k-maps
- $S = (A \oplus B) \oplus C_{in}$
- $C_{out} = AB + (A \oplus B)C_{in}$

$S =$


$ab \backslash c$	0	1
00	0	1
01	1	0
11	0	1
10	1	0

$C_{out} =$

$ab \backslash c$	0	1
00	0	0
01	0	1
11	1	1
10	0	1

Adding 2 Numbers & a Carry (Cont.)


- Draw logic circuit

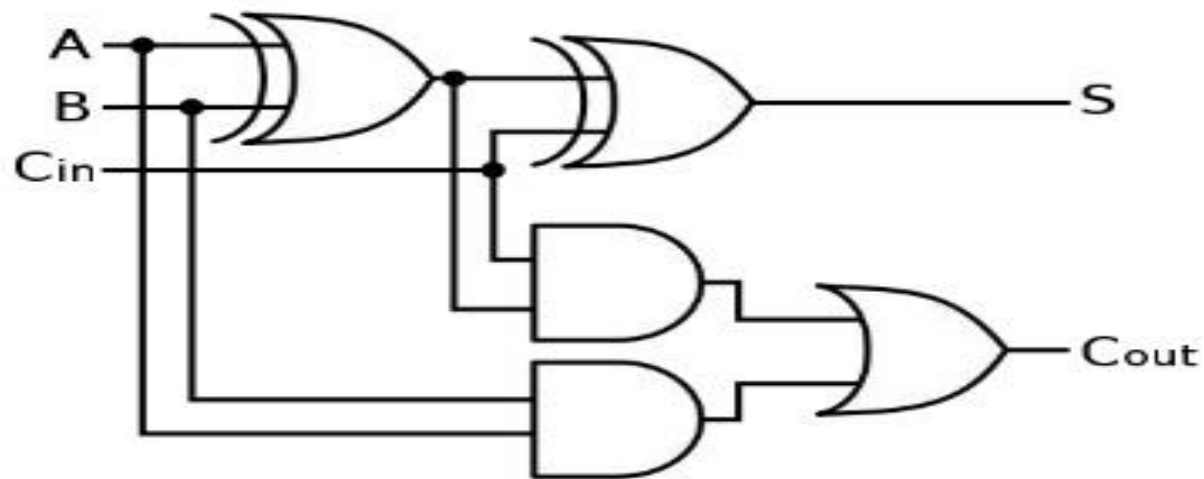

Source: www.setupsolution.com/how-to-design-a-half-adder-and-full-adder-in-verilog-at-gate-level-modeling/


- This is called a full adder

Schematic Representation of Full Adder

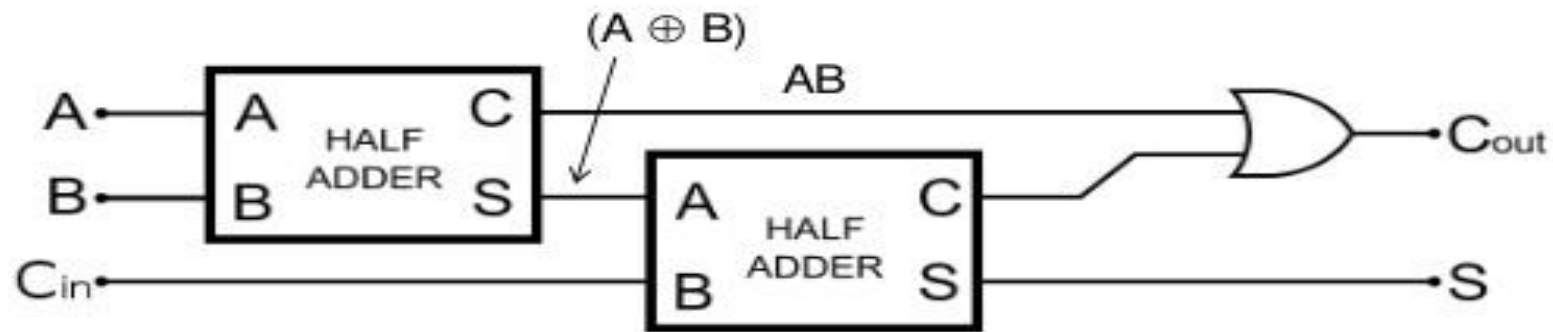

Source: <http://en.wikibooks.org>

n-bit Adder (Ripple Carry Adder)

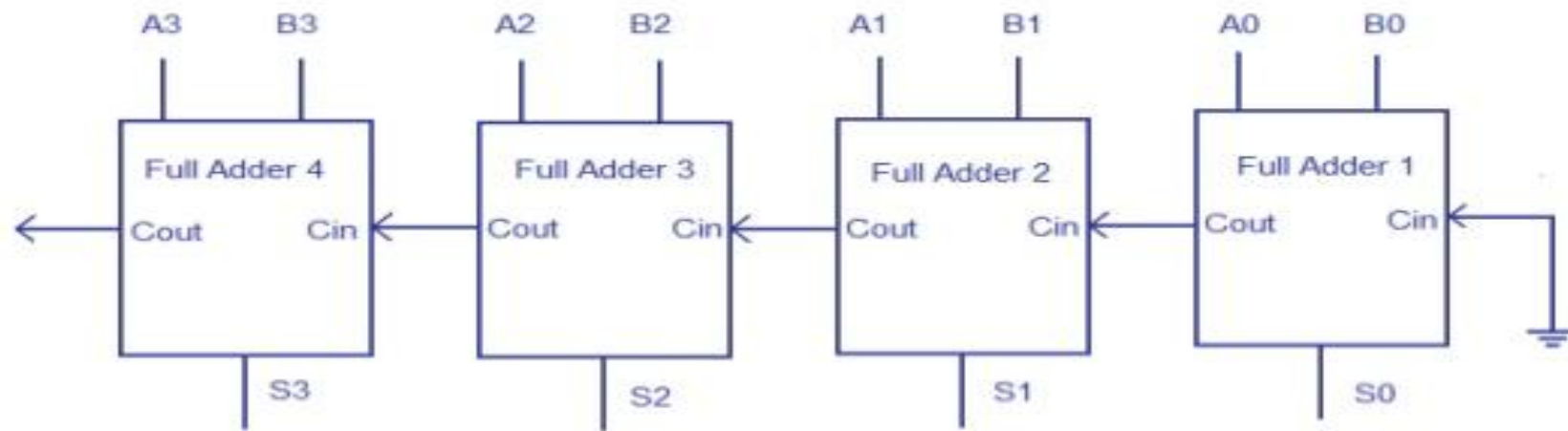


4 bit ripple carry adder

www.circuitstoday.com


SEQUENTIAL LOGIC CIRCUITS

- Made up of combinational circuits and memory elements.
- These memory elements are devices capable of storing ONE-BIT information.
- Output depends on input and previous state.
- Examples of sequential circuits are flip flops, counters, shift registers


BLOCK DIAGRAM OF A SEQUENTIAL CIRCUIT

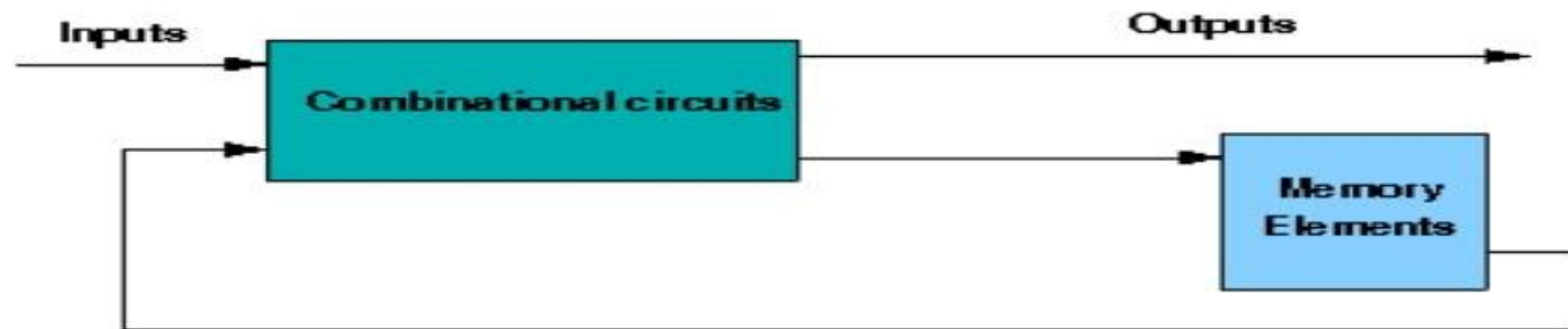

Sequential Logic Circuits Based ALU

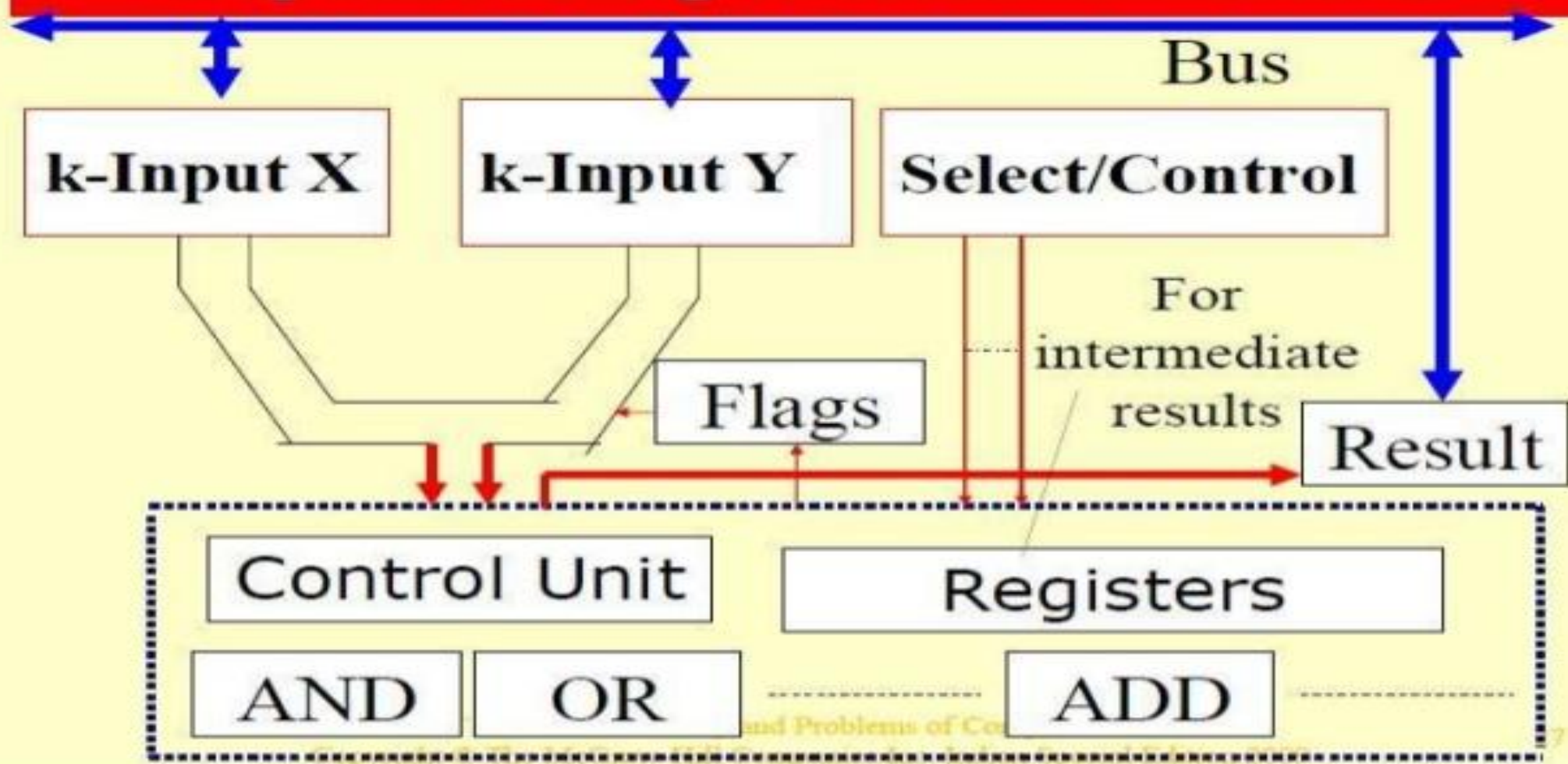

AN ALU USING SEQUENTIAL CIRCUITS

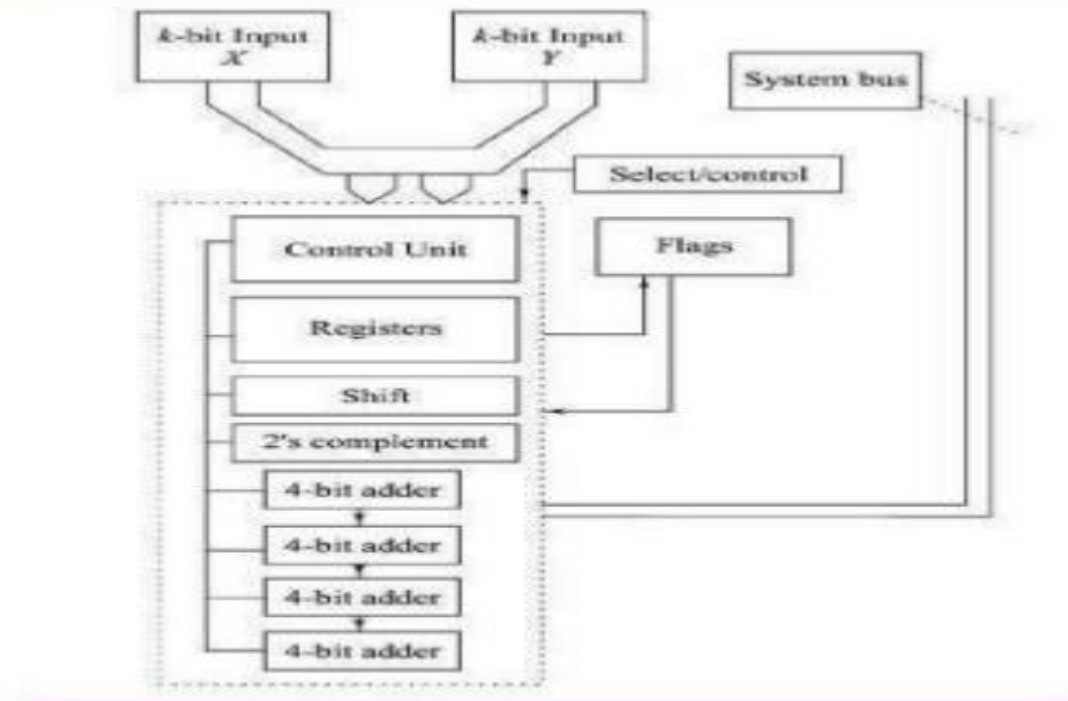

Examples of Sequential Circuits :

- Flip-Flops
 - JK Flip-Flop
 - RS Flip-Flop
 - PR Flip-Flop
 - D Flip-Flop
- Registers
- Counters

Flip-Flops

- Flip-Flops are the basic building blocks of sequential circuits.
- A flip-flop is a binary cell which can store a bit of information.
- A basic function of flip-flop is storage, which means memory. A flip-flop (FF) is capable of storing 1 (one) bit of binary data.
- It has two stable states either '1' or '0'. A flip-flop maintains any one of the two stable states which can be treated as zero or one depending on presence and absence of output signals.

Registers and Counters

- A circuit with flip-flops is considered a sequential circuit even in the absence of combinational logic.
- Circuits that include flip-flops are usually classified by the function they perform.
- Two such circuits are registers and counters:
- **Registers-**
 - It is a group of flip-flops.
 - Its basic function is to hold information within a digital system so as to make it available to the logic units during the computing process.
- **Counters-**
 - It is essentially a register that goes through a predetermined sequence of states.

TYPES OF SEQUENTIAL CIRCUITS

Sequential circuits are of two types:

- *SYNCHRONOUS SEQUENTIAL CIRCUITS*
- *ASYNCHRONOUS SEQUENTIAL CIRCUITS*

→ SYNCHRONOUS CIRCUITS

- In synchronous sequential circuits, the state of the device changes only at discrete times in response to a clock Pulse.
- In a synchronous circuit, an electronic oscillator called a *clock* generates a sequence of repetitive pulses called the *clock signal* which is distributed to all the memory elements in the circuit.

→ ASYNCHRONOUS CIRCUITS

- Asynchronous circuit is not synchronized by a clock signal; the outputs of the circuit change directly in response to changes in Inputs.
- The advantage of asynchronous logic is that it can be faster than synchronous logic, because the circuit doesn't have to wait for a clock signal to process inputs.
- The speed of the device is potentially limited only by the propagation delays of the logic gates used.

THANK YOU

This content is taken from the text books and reference books prescribed in the syllabus.